

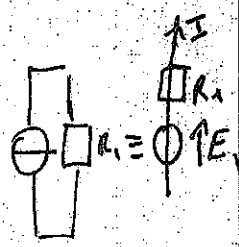


Exercício II

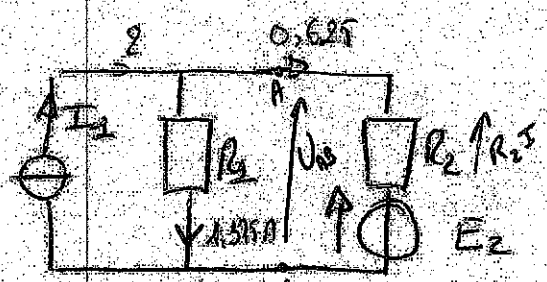

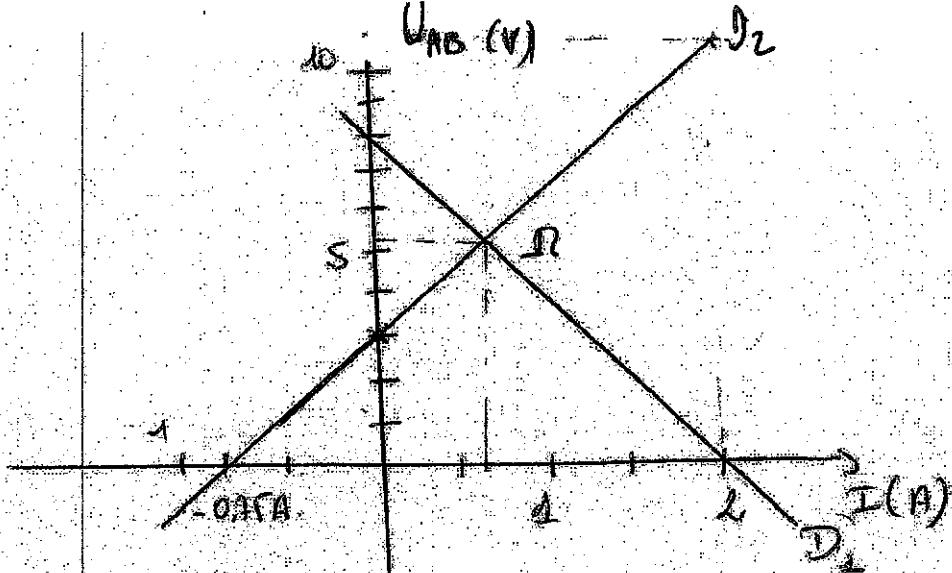par D_1 :
 $I_{cc} = 2A$ $R_2 = 4\Omega$
 $E_1 = 8V$
 $U_{AB} = E_1 - R_2 I$
 par D_2
 $I_{cc} = 3A$
 $E_2 = 3V$ $R_2 = 4\Omega$
 $U_{AB} = E_2 + R_2 I$



$$E_1 - R_1 I = E_2 + R_2 I$$

$$I = \frac{E_1 - E_2}{R_1 + R_2} = \frac{8 - 3}{8} = \frac{5}{8} = 0,625 \text{ A.}$$

$$U_{AB} = E_2 + R_2 I = 3 + 2,5 = 5,5 \text{ V.}$$

	Current:	I (A)	U (V)	P (W)	function	
3)	D_1	generator	0,625	5,5	3,44	generator
	D_2	receptor	0,625	5,5	3,44	receptor
4)	I_1	generator	2	5,5	11	generator
	R_1	receptor	1,625	5,5	2,56	receptor
	R_2	receptor	0,625	2,5	1,56	receptor
	E_2	receptor	0,625	3	1,88	receptor

$$\sum P_{consumes} = \sum P_{sources}$$