

~~Ex 9~~

$$1) U_{AB} = \frac{R R_2 E_1}{R_1 + \frac{R R_2}{R + R_2}} - \frac{R R_1 E_2}{R_2 + \frac{R R_1}{R + R_1}} = \frac{R R_2 E_1}{R_1 R + R_1 R_2 + R R_2} - \frac{R R_1 E_2}{R_2 R + R_1 R_2 + R R_1}$$
$$= \frac{R (R_2 E_1 - R_1 E_2)}{R_1 R_2 + R_1 R + R_2 R}$$

on met un fil \Rightarrow possible
1 des gènes
(circuit-circuit)

AN: $U_{AB} = \frac{10 (15 \times 20 - 10 \times 12)}{10 \times 15 + 10 \times 10 + 15 \times 10} = 4,5 \text{ V}$

2) Thévenin en prenant $V_B = 0 \Rightarrow$ application directe

$$V_A = \frac{E_1}{\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2}} - \frac{E_2}{R_2} = \frac{R (R_2 E_1 - R_1 E_2)}{R_1 R_2 + R R_1 + R R_2} = 4,5 \text{ V}$$