

1

I₁ a) $R_{AN} = R_1 + R_2 + R_3 + R_4$ (1) $si R_{0,5}$

b) $E = (R + R_{AN}) I$

$I = \frac{E}{R + R_{AN}}$ $U = \frac{RE}{R + R_1 + R_2 + R_3 + R_4}$ (1,5)


2.

| k_1 | k_2 | k_3 | k_4 | R_{AN} | U |
|-------|-------|-------|-------|----------|--------|
| 0 | 0 | 0 | 0 | 4 kΩ | 1 V |
| 1 | 0 | 0 | 0 | 0 | 5 V |
| 0 | 1 | 0 | 0 | 1 kΩ | 2,5 V |
| 0 | 0 | 1 | 0 | 2 kΩ | 1,67 V |
| 0 | 0 | 0 | 1 | 3 kΩ | 1,2 V |



(2,5)

1 si out connect.

II 1.

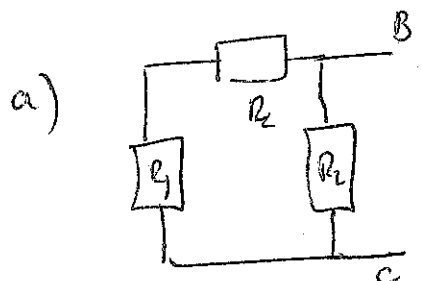

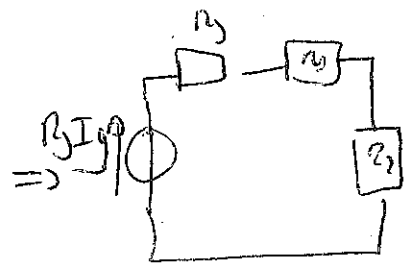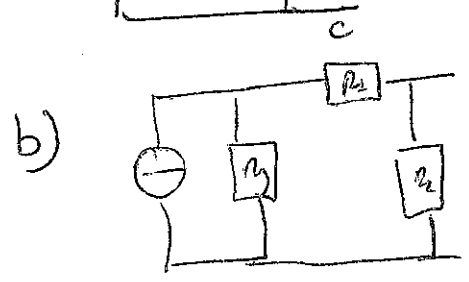$R_{th} = \frac{R_2 (R_3 + R_4)}{R_2 + R_3 + R_4}$ (2)




$E_{th} = \frac{R_2 R_3 I_g}{R_2 + R_3 + R_4}$ (2)

II a) $I = \frac{E_{th}}{R_{th} + R}$ (1)

b) $I = \frac{\frac{R_2 R_3 I_g}{R_2 + R_3 + R_4}}{R + \frac{R_2 (R_3 + R_4)}{R_2 + R_3 + R_4}} = \frac{R_2 R_3 I_g}{R (R_2 + R_3 + R_4) + R_2 (R_3 + R_4)}$ (2)

III-1. you permit.

(2)

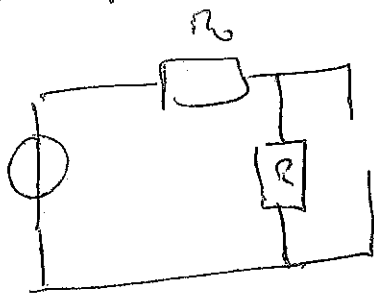

$$u = \frac{R}{R_0 + R} E$$

$$i_c = 0$$

$$i_R = \frac{E}{R + R_0}$$

$$i = i_R$$

$$10 = 0.05$$

III-2 à $t \geq 0^+$, continuité de la tension aux bornes de C $u_c = 0$ 0.05

$$\Rightarrow i_R(t=0) = 0; \quad i_c(t=0) = \frac{E}{R_0} \quad 10$$

III-3 $u = R i_R \xleftrightarrow{0.05 \text{ you derive}} i_c = C \frac{du}{dt}$

$$i_c = RC \frac{di_R}{dt} \quad 10$$

III-4. $E - R_0 i - R i_R = 0$

$$E - R_0 i_R - R_0 i_c - R i_R = 0$$

$$(R_0 + R) i_R + R_0 i_c = E$$

$$(R_0 + R) i_R + R_0 RC \frac{di_R}{dt} = E$$

$$\frac{di_R}{dt} + \frac{R_0 + R}{R_0 RC} i_R = \frac{E}{R_0 RC}$$

$$\tau = \frac{R_0 RC}{R_0 + R}$$

S- $i_{Rp} = \frac{E}{R_0 + R}$ $i_{RH} = A e^{-\frac{t}{\tau}}$

à $t=0$, $i_R = 0 \Rightarrow i_R = \frac{E}{R_0 + R} (1 - e^{-\frac{t}{\tau}})$

(1)

3

$$i_c = RE \frac{di_R}{dt} = \frac{RE}{R_0 + R} \frac{1}{G} e^{-\frac{t}{G}}$$

$$i_c = \frac{RE}{R_0 + R} \frac{R_0 + R}{R_0 RE} e^{-\frac{t}{G}}$$

$$i_c = \frac{E}{R_0} e^{-\frac{t}{G}} \quad (0.15)$$

$$i = i_c + i_R = \frac{E}{R_0} e^{-\frac{t}{G}} + \frac{E}{R_0 + R} (1 - e^{-\frac{t}{G}}) \quad (0.15)$$

