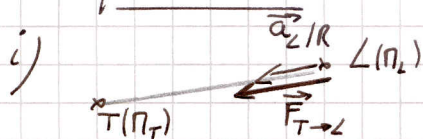


## Questions de cours



ii) RFD  $\vec{a}_L = \frac{v_L^2}{r_L} \vec{e}_m$  (pas de composante tangentielle)

$$\vec{F}_{T \rightarrow L} = -G \frac{m_T m_L}{r_L^2} \frac{\vec{T}L}{TL} = G \frac{m_T m_L}{r_L^2} \vec{e}_m$$

$$M_L \vec{a}_{L/R} = \sum \vec{F}_{ext} \text{ donne } \frac{m_L v_L^2}{r_L} = G \frac{m_T m_L}{r_L^2}$$

$$\text{soit } v_L = \sqrt{\frac{G m_T}{r_L}}$$

iii) identité masse grave  $\equiv$  masse inerte  $\checkmark$  AN  $v_L = 1,020 \text{ km/s}$

Problème  $R = 100 \Omega$ ,  $L = 10 \text{ mH}$ ,  $C = 0,5 \mu\text{F}$

$$e(t) = e_m \cos(\omega t + \phi_e) \Rightarrow i(t) = i_m \cos(\omega t + \phi_i)$$

- 1)  $e_m$ : amplitude tension (V)  
 $i_m$ : amplitude courant (A)  
 $\phi_e, \phi_i$ : phase origine (rad)  
 $\omega$ : pulsation ( $\text{rad}\cdot\text{s}^{-1}$ )


2) a)  $u_R(t) = R i(t)$

$$u_L(t) = L \frac{di(t)}{dt}$$

$$u_C(t) = \frac{1}{C} \int i(t) dt$$

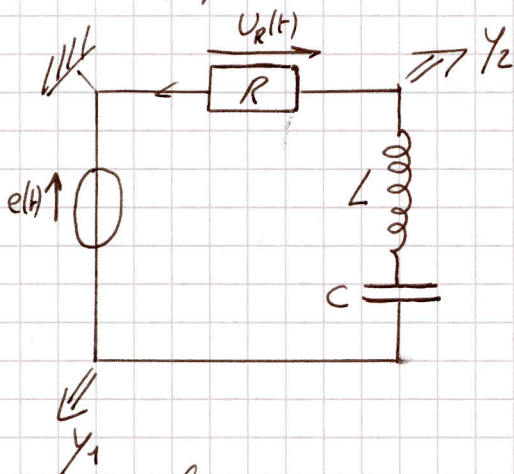b)  $e(t) = u_R(t) + u_L(t) + u_C(t)$  soit  $R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt = e(t)$

$u_R(t)$  est proportionnel au courant  $u_R(t) = R i(t) \rightarrow i(t) = \frac{u_R(t)}{R}$



3) Formalisme complexe a)  $e(t) = e_m \cos(\omega t + \phi_e) \Rightarrow \underline{e}(t) = e_m e^{j\omega t}$  avec  $e_m = e_m e^{j\phi_e}$   
 $i(t) = i_m \cos(\omega t + \phi_i) \Rightarrow \underline{i}(t) = i_m e^{j\omega t}$  avec  $i_m = i_m e^{j\phi_i}$

b) Equation complexe en  $\underline{i}(t)$

$$R \underline{i}(t) + L \frac{d\underline{i}(t)}{dt} + \frac{1}{C} \int \underline{i}(t) dt = \underline{e}(t)$$

②

c)  $\frac{d\underline{i}(t)}{dt} = j\omega \underline{i}_m e^{j\omega t}$

$$\int \underline{i}(t) dt = \frac{1}{j\omega} \underline{i}_m e^{j\omega t} = -\frac{j}{\omega} \underline{i}_m e^{j\omega t}$$

d)  $R \underline{i}_m + jL\omega \underline{i}_m - \frac{j}{C\omega} \underline{i}_m = \underline{e}_m \Rightarrow \underline{i}_m = \frac{\underline{e}_m}{R + j(L\omega - \frac{1}{C\omega})}$

4) a)  $Z_R = R$  ;  $Z_L = jL\omega$  ;  $Z_C = \frac{1}{jC\omega} = \frac{-j}{C\omega}$

$$Z = Z_R + Z_L + Z_C = R + j(L\omega - \frac{1}{C\omega})$$

Module  $\Rightarrow |Z| = \sqrt{R^2 + (L\omega - \frac{1}{C\omega})^2}$

Argument  $\Rightarrow \phi_z = \arg Z = \arctan\left(\frac{L\omega - \frac{1}{C\omega}}{R}\right)$

b)  $\underline{Y} = \frac{\underline{i}(t)}{\underline{e}(t)} = \frac{1}{Z} = \frac{1}{R + j(L\omega - \frac{1}{C\omega})}$  car  $\underline{e}(t) = Z \underline{i}(t)$

Module  $\Rightarrow |\underline{Y}| = \frac{1}{\sqrt{R^2 + (L\omega - \frac{1}{C\omega})^2}} = \frac{1}{|Z|}$

Argument  $\Rightarrow \phi_Y = \arg \underline{Y} = -\arctan\left(\frac{L\omega - \frac{1}{C\omega}}{R}\right) = -\phi_z$

c)  $\omega = \omega_0 \Rightarrow |\underline{Y}|_{\max} = \frac{1}{R}$   $L\omega_0 = \frac{1}{C\omega_0} \Leftrightarrow \omega_0 = \frac{1}{\sqrt{LC}}$   
*résonance.*

5) Fonction de transfert  $\underline{T}(f) = \frac{U_R(t)}{\underline{e}(t)} = \frac{R \underline{i}(t)}{Z \underline{i}(t)} = \frac{R}{Z} = \frac{R}{R + j(L\omega - \frac{1}{C\omega})}$

Facteur de qualité  $Q = \frac{L\omega_0}{R} \text{ et } x = \frac{\omega}{\omega_0}$   
 $\omega_0 = 14,142 \cdot 10^3 \text{ rad/s}$   
 AN:  $Q = 1,414$

$$= \frac{1}{1 + j\left(\frac{L\omega}{R} - \frac{1}{RC\omega}\right)} = \frac{1}{1 + j\left(\frac{L\omega_0}{R} \frac{\omega}{\omega_0} - \frac{1}{RC\omega_0} \frac{\omega_0}{\omega}\right)} = \frac{1}{1 + j\left(Qx - \frac{1}{Qx}\right)} = [1 + jQ\left(x - \frac{1}{x}\right)]^{-1}$$

6) Gain G a)  $G(\text{dB}) = 20 \text{ P}_g |T(x)| = 20 \text{ P}_g \left[ \frac{1}{1 + Q^2 \left(x - \frac{1}{x}\right)^2} \right]^{\frac{1}{2}} = -10 \text{ P}_g [1 + Q^2 \left(x - \frac{1}{x}\right)^2]$

b) Echelle log  $\Rightarrow$  large domaine spectral  $X=0 \quad G=0$  (valeur max) | filtre passe-bande  
 $=+\infty \quad +20X$